

Electric Current

$$i = q/t$$

1 Coulomb = Ampere sec.  
 1 amp =  $6.25 \times 10^{18}$  electrons


t = 1 sec      q - amount      Amperes

D C



straight line.  
NO fluctuation


A C

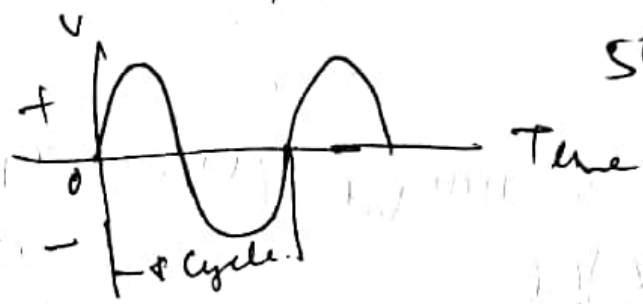

Electric Resistance

$$R = \frac{V}{i}$$

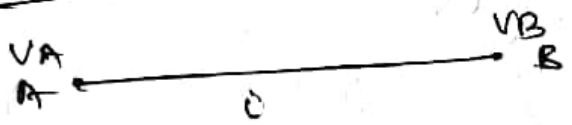Unit:  $\frac{\text{volts}}{\text{amp}} = \frac{\text{ohm}}{\text{amp}}$   
mks       $\Omega$  unit



Law of Resistance

$$R \propto l$$

$$R \propto \frac{1}{A}$$

Area Cross sectional  
Area of wire

$$R \propto \frac{l}{A}$$

Ohm's Law


$$\frac{V}{i} = \text{const}$$

$$\frac{V}{i} = R$$


$$i \propto V$$

$$V \propto i$$

$$V = Ri$$

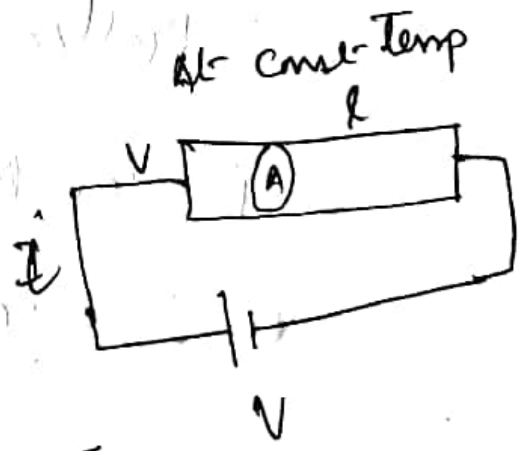


Resistance (Resistance)  
Ohm  $\Omega$

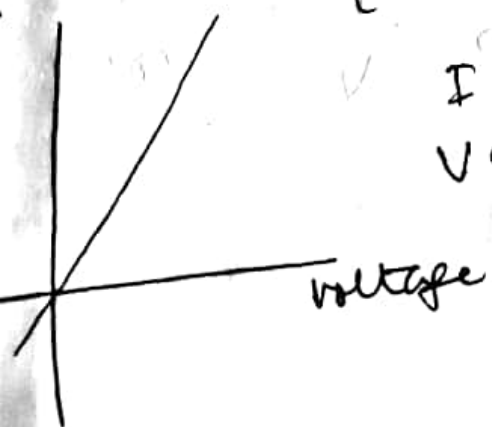
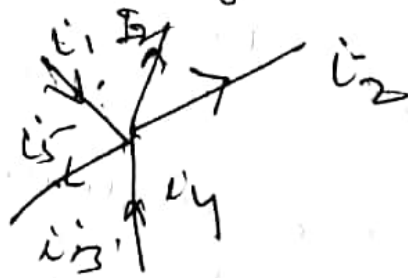
# Kirchoff's Laws ← KCL KVL

In any network of conductors, the algebraic sum of currents meeting at a point is zero


$i_1$  &  $i_4$  are +ve current  
 $i_2, i_3, i_5$



$$i_1 + i_4 = i_2 + i_3 + i_5$$

$$i_1 - i_2 + i_4 - i_3 - i_5 = 0$$

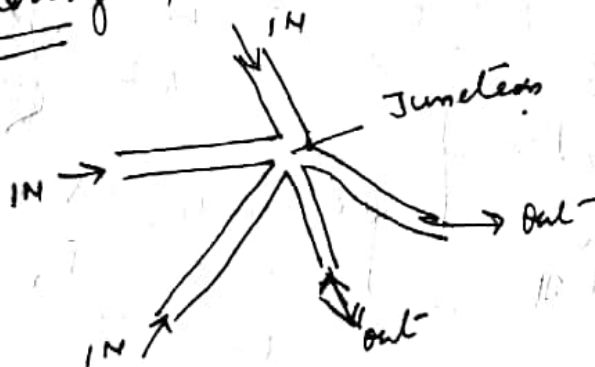In simple way, we can say total current leaving a junction is equal to the total current entering that junction.



$$I_{in} = I_{out}$$

$$I_{in} - I_{out} = 0$$

## Kirchoff's Voltage Law

The algebraic sum of all IR drops and EMFs in any closed loop of a network is zero.

$$\sum IR = \sum EMF = 0$$

→ Increase in voltage (IR) would be considered +ve.


→ fall in voltage (IR) would be taken as -ve.

Second point is → if we go from -ve terminal to +ve terminal of BTY there is rise in potential, hence Emf will be +ve & vice versa.

Contd to KVL

if we go in the direction of current, there is fall of voltage since current always flows from higher to a lower potential. so -ive (IR)

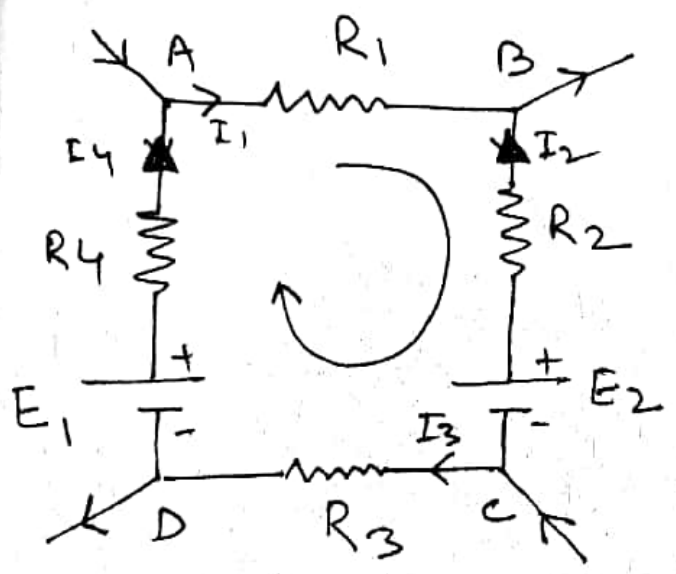if we go against current direction. it means we are coming from low potential to high potential so IR will be +ive.



ABC D is a closed loop

if we go in clockwise direction.

- $I_1 R_1 \rightarrow$  -ive (fall of potential)
- $I_2 R_2 \rightarrow$  +ive (rise - - -)
- $E_2 \rightarrow$  -ive. (fall - - -)
- $I_3 R_3 \rightarrow$  -ive (- - -)
- $E_1 \rightarrow$  +ive (rise - -)
- $I_4 R_4 \rightarrow$  -ive. (fall - -)

Hence according to KVL

$$- I_1 R_1 + I_2 R_2 - E_2 - I_3 R_3 + E_1 - I_4 R_4 = 0$$

$$- I_1 R_1 + I_2 R_2 - I_3 R_3 - I_4 R_4 = E_2 - E_1$$

~~if we go~~ In Anti clockwise

DCBA


$$I_4 R_4 - I_3 R_3 - E_1 + I_3 R_3 + E_2 - I_2 R_2 + I_1 R_1 = 0$$

$$I_4 R_4 + I_3 R_3 - I_2 R_2 + I_1 R_1 = E_1 - E_2$$

# Combinations of Resistances

## In Series

Current passes through  $R_1, R_2, R_3$

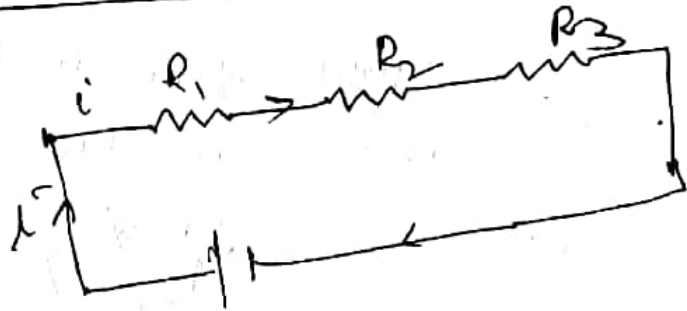

$i$  is same.

But - voltage is different

$$V = iR$$

$$V_1 = i R_1 \quad V_3 = i R_3$$

$$V_2 = i R_2$$


$$V = V_1 + V_2 + V_3$$

$$V = iR_1 + iR_2 + iR_3$$

$$iR = i(R_1 + R_2 + R_3)$$

$$R = R_1 + R_2 + R_3$$

## Parallel

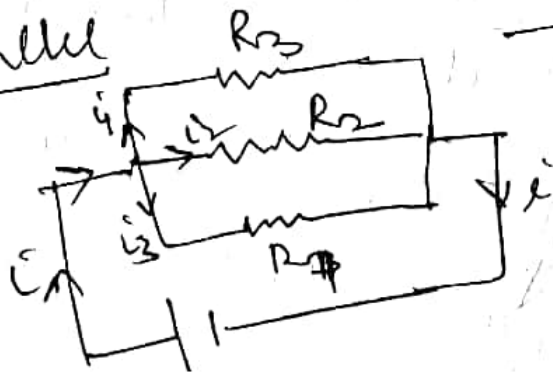

$$i = \frac{V}{R}$$

$$i_1 = \frac{V}{R_1}$$

$$i_2 = \frac{V}{R_2} \quad i_3 = \frac{V}{R_3}$$

$$i = i_1 + i_2 + i_3$$

$$\frac{V}{R} = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$